



Sanjay Ghodawat University, Kolhapur

Established as State Private University under Govt. of Maharashtra. Act No XL, 2017

2018-19

EXM/P/09/01

Year and Program: 2018-19
Electrical & Electronics
Course Code: EET 206

School of Technology

Course Title: Digital Electronics

Department of Electrical & Electronics
SY B.Tech
Semester - II

Day and Date Saturday
25-05-2019

End Semester Examination
(ESE)

Time: 3 Hrs. Max Marks: 100
10.30 am to 1.30 pm

Instructions:

- 1) All questions are compulsory.
- 2) Assume suitable data wherever necessary.
- 3) Figures to the right indicate full marks.

Q.1	Solve the following.	Marks	Bloom's Level	CO
a)	List all characteristics of Digital ICs. Explain in Details any three.	07	L1	CO1
OR				
a)	Compare CMOS & TTL Logic Family	07	L4	CO1
b)	State and prove associative, commutative, Distributive and Negation Laws of Boolean algebra.	08	L3	CO2
OR				
b)	Write short notes on Demorgan's Theorem. Solve $\overline{(\overline{A+B})}(\overline{A+B})$	08	L3	CO2
Q.2	Solve the following.			
a)	Differentiate between SOP and POS form. Write Minterm & Maxterm for 3 (A,B,C) variable.	07	L3	CO3
OR				
a)	Reduce the expression $F = \sum m(0,2,3,4,5,6)$ using K-mapping & implement it in AOI Logic as well as in NAND Logic.	07	L4	CO3
b)	Explain Full Adder & implement it using 2 Half Adder.	08	L3	CO4
OR				
b)	Design a 4-Bit Binary to Gray Code converter.	08	L4	CO4

ESE

Page 1/2

Q.3	Solve any Two			
a)	Prove that 1. $A\bar{B}C+B+B\bar{D}+AB\bar{D}+\bar{A}C=B+C$	08	L3	CO1
	2. $AB+\bar{A}C=(A+C)(\bar{A}+B)$			
b)	Explain 2-Bit and 4-bit Magnitude comparator.	08	L3	CO2
c)	Solve equation using Quine McCluskey method. $F(A,B,C,D)=\sum m(0,2,3,6,7,8,10,12,13)$	08	L3	CO3
d)	Design the following logic function using 8:1 MUX $F(A,B,C,D)=\sum m(1,3,4,11,12,13,14,15)$.	08	L3	CO4
Q.4	Solve any Two			
a)	Design and implement edge triggered D-flip flop.	09	L3	CO5
b)	What is the shift register? Explain Parallel In Serial Out shift Register.	09	L3	CO5
c)	Design 4-bit UP Ripple counter by using T-flip flops.	09	L3	CO5
Q.5	Solve any Two			
a)	Explain Moore and Mealy machines in detail.	09	L3	CO5
b)	Explain State Diagram, State Table, State Assignment and State Reduction Techniques.	09	L2	CO5
c)	Explain in detail universal shift register.	09	L4	CO5
Q.6	Solve any Three			
a)	Compare combinational and sequential Logic Circuits.	06	L3	CO5
b)	Convert S-R flip-flop to J-K flip-flop.	06	L3	CO5
c)	Design MOD-6 Asynchronous counter using T flip-flops.	06	L4	CO5
d)	Explain about the twisted Ring counter (Johnson Counter).	06	L2	CO5

ESE

Page 2/2